

Phy 112

Name : Uday Saha

ID : 21301095

Section : 10

Chapter 25, Problem 53

Here, plate area, $A = 0.12 \text{ m}^2$

Separation distance, $d = 1.2 \text{ cm} = 0.012 \text{ m}$

Potential difference, $V = 120 \text{ V}$

Thickness of dielectric slab, $b = 4 \text{ mm} = 4 \times 10^{-3} \text{ m}$

Dielectric constant, $k = 4.8$

a)

Capacitance before the slab is inserted,

$$C_0 = \frac{\epsilon_0 A}{d} = \frac{8.854 \times 10^{-12} \times 0.12}{0.012}$$

$$= 8.854 \times 10^{-11} \text{ F}$$

(Ans)

b)

Capacitance with the slab in place,

$$C = \frac{\epsilon_0 A}{d - b + \frac{b}{k}} = \frac{8.854 \times 10^{-12} \times 0.12}{0.012 - (4 \times 10^{-3}) + \frac{4 \times 10^{-3}}{4.8}}$$

$$= 1.2 \times 10^{-10} \text{ F}$$

(Ans)

c)

Free charge before slab is inserted,

$$q_0 = C_0 V = 8.854 \times 10^{-11} \times 120$$

$$= 1.06248 \times 10^{-8} \text{ C}$$

(Ans)

[d] Free charge after the slab inserted,

$$q = q_0 = 1.06248 \times 10^{-8} \text{ C} \quad (\text{Ans})$$

Because, the battery is disconnected.

[e] Magnitude of the electric field in the space between the plates and the dielectric,

$$E_0 = \frac{q_0}{\epsilon_0 \cdot A} = \frac{1.06248 \times 10^{-8}}{8.854 \times 10^{-12} \times 0.12} = 10^4 \text{ V m}^{-1} \quad (\text{Ans})$$

[f] Magnitude of the electric field in the dielectric,

$$E = \frac{E_0}{K} = \frac{10^4}{4.8} = 2083.33 \text{ V m}^{-1} \quad (\text{Ans})$$

[g] Potential difference across the plates,

$$\begin{aligned} V &= E_0 (d - b) + E b \\ &= 10^4 (0.012 - 4 \times 10^{-3}) + 2083.33 \times 4 \times 10^{-3} \\ &= 883.33 \text{ V} \end{aligned}$$

$$0.51 \times 10^{-1} \times 1.06248 \times 10^{-8} = V_0 \cdot C = 0.9$$
$$0.8 - 0.1 \times 0.8520 \cdot 1 =$$

(A) External work done to insert the slab,

$$W_{\text{ext}} = \Delta U = U_f - U_i = \frac{q^2}{2C} - \frac{q_0^2}{2C_0}$$

$$= \frac{q^2}{2} \left(\frac{1}{C} - \frac{1}{C_0} \right)$$

$$= \frac{(1.06248 \times 10^{-8})^2}{2} \left(\frac{1}{1.2 \times 10^{-10}} - \frac{1}{8.854 \times 10^{-12}} \right)$$

$$= -1.67 \times 10^{-7} \text{ J}$$

(Ans)

Chapter 26 : Problem 16

Here,

$$I = 60 \text{ A}$$

$$\frac{R}{L} = 0.150 \frac{\Omega}{\text{km}} = \frac{\sigma}{A}$$

(C) For copper cable, $J = \frac{I}{A} = \frac{I \times (0.150 \div 1000)}{\sigma}$

$$= \frac{60 \times (0.150 \div 1000)}{1.77 \times 10^{-8}}$$

$$= 508475 \times 10^{-6} \text{ A/m}^2$$

$$\text{Total current density of each} = 508.475 \times 10^3 \text{ A m}^{-2}$$

$$\frac{V}{0.95} - \frac{V}{0.95} = ; V = V \quad (\text{Ans})$$

$$\left(\frac{1}{0.95} - \frac{1}{0.95} \right) \frac{V}{0.95}$$

b For copper, mass per unit length,

$$\lambda = \frac{m}{L} = \rho A = \rho \cdot \frac{\pi}{(0.150 \div 1000)}$$

(Ans)

$$= 8960 \times \frac{1.77 \times 10^{-8}}{(0.150 \div 1000)}$$

$$= 1.05728 \text{ kg m}^{-1} \quad (\text{Ans})$$

c For Aluminum cable,

$$J = \frac{I}{A} = \frac{I \times (0.150 \times 1000)}{\pi} = \frac{60 \times 0.15 \times 10^{-3}}{2.65 \times 10^{-8}}$$

$$= 339.623 \times 10^3 \text{ A m}^{-2}$$

(Ans)

$$\frac{V}{A} = \frac{1.01}{0.120} = \frac{V}{I}$$

d For Aluminum, $\lambda = \frac{m}{L} = \rho A = \rho \cdot \frac{\pi}{(0.15 \times 10^{-3})}$

$$= \frac{I}{A} = \frac{60}{2.65 \times 10^{-8}} = 2600 \times \frac{2.65 \times 10^{-8}}{0.15 \times 10^{-3}}$$

$$= 0.4593 \text{ kg m}^{-1}$$

(Ans)

Chapter 27 : Problem 23


Here, $R_1 = 100 \Omega$

$R_2 = 50 \Omega$

$\mathcal{E}_1 = 6 \text{ V}$

$\mathcal{E}_2 = 5 \text{ V}$

$\mathcal{E}_3 = 4 \text{ V}$

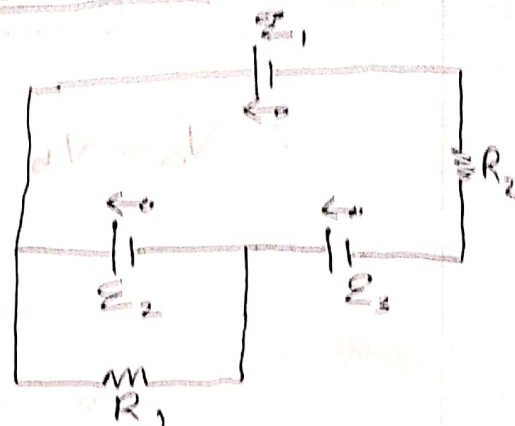


a For the lower loop, let the electron flow for R_1 be from left to right.

\therefore According to KVL,

$$\mathcal{E}_2 - i_1 R_1 = 0$$

$$i_1 = \frac{\mathcal{E}_2}{R_1} = \frac{5}{100} = 0.05 \text{ A}$$

(Ans)

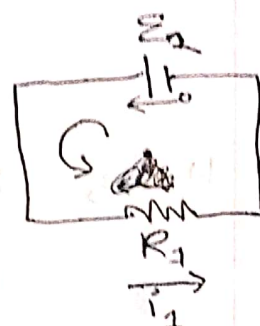


b For the upper loop, let the current flow for R_2 be from top to bottom.


\therefore According to KVL,

$$-\mathcal{E}_1 - i_2 R_2 + \mathcal{E}_3 + \mathcal{E}_2 = 0$$
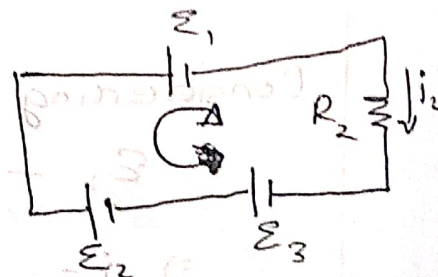
$$\therefore i_2 = \frac{\mathcal{E}_2 + \mathcal{E}_3 - \mathcal{E}_1}{R_2} = \frac{5 + 4 - 6}{50} = 0.06 \text{ A}$$



(c)

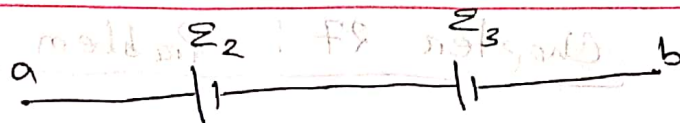

$$\therefore V_a - V_b = \varepsilon_3 + \varepsilon_2 = 4 + 5 = 9 \text{ V}$$

(Ans.)

$$V_a - V_b = 9 \text{ V}$$


Chap 27 : Problem 31

Here,

$$\varepsilon_1 = 5 \text{ V}$$

$$\varepsilon_2 = 12 \text{ V}$$

Each resistor has, $R = 2 \Omega$

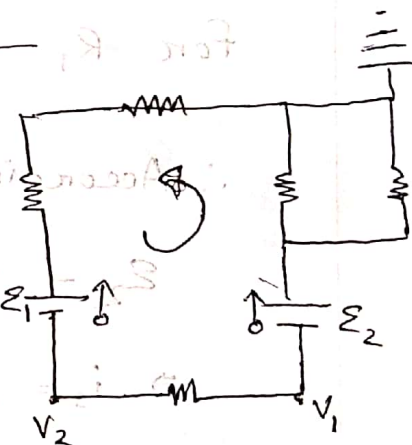

$$\therefore R_{eq} = R + R + \left(\frac{1}{R} + \frac{1}{R} \right)^{-1} + R$$

$$= 3R + \frac{R}{2} = 3 \times 2 + \frac{2}{2} = 7 \Omega$$

Considering the current flow to be clockwise,


$$\varepsilon_1 - i R_{eq} - \varepsilon_2 = 0$$

$$\Rightarrow i = \frac{\varepsilon_1 - \varepsilon_2}{R_{eq}} = \frac{5 - 12}{7} = -1 \text{ A}$$

$\therefore |i| = 1 \text{ A}$, which flows anti-clockwise

[a] Here, resistance of only the parallel connection,
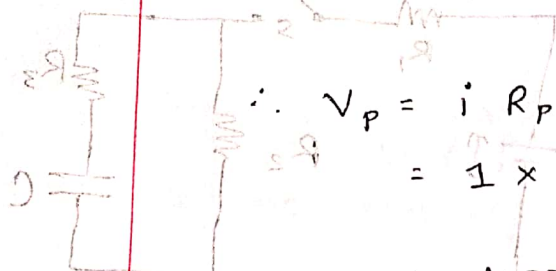
$$R_p = \left(\frac{1}{R} + \frac{1}{R} \right)^{-1} = 1 \Omega$$



$$\therefore V_p = i R_p$$

$$= 1 \times 1 = 1 \text{ V}$$

\therefore Potential difference between Ground and ~~V1~~ V_1 ,

$$V_0 - V_1 = \varepsilon_2 - V_p$$

$$\Rightarrow 0 - V_1 = 12 - 1$$

$$\therefore V_1 = -11 \text{ V}$$

(Ans)

[b] Potential difference between Ground and V_2 ,

$$V_2 - V_0 = -iR - iR - \varepsilon_1$$

$$\Rightarrow V_2 - 0 = -2 \times 1 \times 2 - 5$$

$$\therefore V_2 = -9 \text{ V}$$

$$V_0 - V_2 = \left(\frac{1}{R} + \frac{1}{R} \right)^{-1} = 1 \Omega \quad \text{(Ans)}$$


Chapter 27 : Problem 63

Here, $\mathcal{E} = 1.2 \text{ kV}$
 $= 1.2 \times 10^3 \text{ V}$

$C = 6.5 \mu\text{F}$

$C = 6.5 \times 10^{-6} \text{ F}$

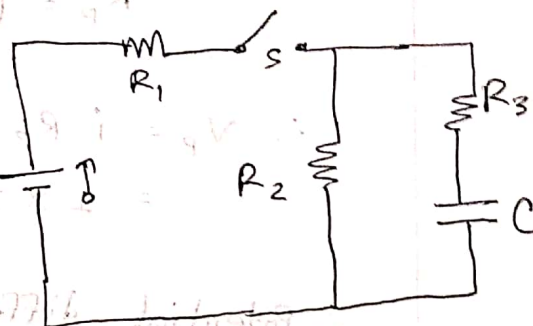$R_1 = R_2 = R_3 = 0.73 \text{ M}\Omega$
 $= 0.73 \times 10^6 \Omega$



At $t = 0$, the capacitor will be uncharged and we can take the equivalent resistance from the circuit ignoring the capacitor.

$\therefore R_{eq} = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 1.095 \times 10^6 \Omega$

[a] At $t = 0$, $i_1 = \frac{\mathcal{E}}{R_{eq}} = 1.096 \times 10^{-3} \text{ A}$ (Ans)

[b] Here, $i_p = i_1 = 1.096 \times 10^{-3} \text{ A}$

$\therefore V_p = i_p \times R_p = i_p \times \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 400 \text{ V}$

Therefore, $i_2 = \frac{V_p}{R_2} = 5.479 \times 10^{-4} \text{ A}$ (Ans)

$$\text{c)} \quad i_3 = \frac{V_P}{R_3} = \frac{V_P}{R_2} = i_2 = 5.479 \times 10^{-4} \text{ A} \quad (\text{Ans})$$

Now, at $t = \infty$, the capacitor will be fully charged.
So, no current will pass through R_3 and C .

d) When $t = \infty$ s,

$$i_1 = \frac{\mathcal{E}}{R_5} = \frac{1.2 \times 10^3}{2(6.73 \times 10^6)} = \cancel{1.64 \times 10^{-4} \text{ A}} \\ = 8.219 \times 10^{-4} \text{ A} \quad (\text{Ans})$$

$$\text{e)} \quad i_2 = \frac{\mathcal{E}}{R_5} = i_1 = 8.219 \times 10^{-4} \text{ A} \quad (\text{Ans})$$

f) As no current will pass through R_3 ,

$$i_3 = 0 \text{ A} \quad (\text{Ans})$$

At any time t , for the left loop, $\mathcal{E} - i_1 R_1 - i_2 R_2 = 0$
for the right loop, $-i_3 R_3 - V_C + i_2 R_4 = 0$

(g) At $t = 0$ s, $i_2 = \frac{V_2}{R_2} = \frac{400}{80} = 5 \text{ A}$ [2]

$$i_2 = 5.479 \times 10^{-4} \text{ A}$$

V_2 at $t = 0$ s is, $V_2 = i_2 R_2$
 $= 400 \text{ V}$ (Ans)

(h) At $t = \infty$ s, $i_2 = \frac{3}{2} = 1.5 \text{ A}$ [2]

$$i_2 = 8.219 \times 10^{-4} \text{ A}$$

V_2 at $t = \infty$ s is, $V_2 = i_2 R_2$
 $= 600 \text{ V}$

$A \times 0.1 \times 0.15 \times 8 = i = \frac{3}{2} = 1.5 \text{ A}$ (Ans)

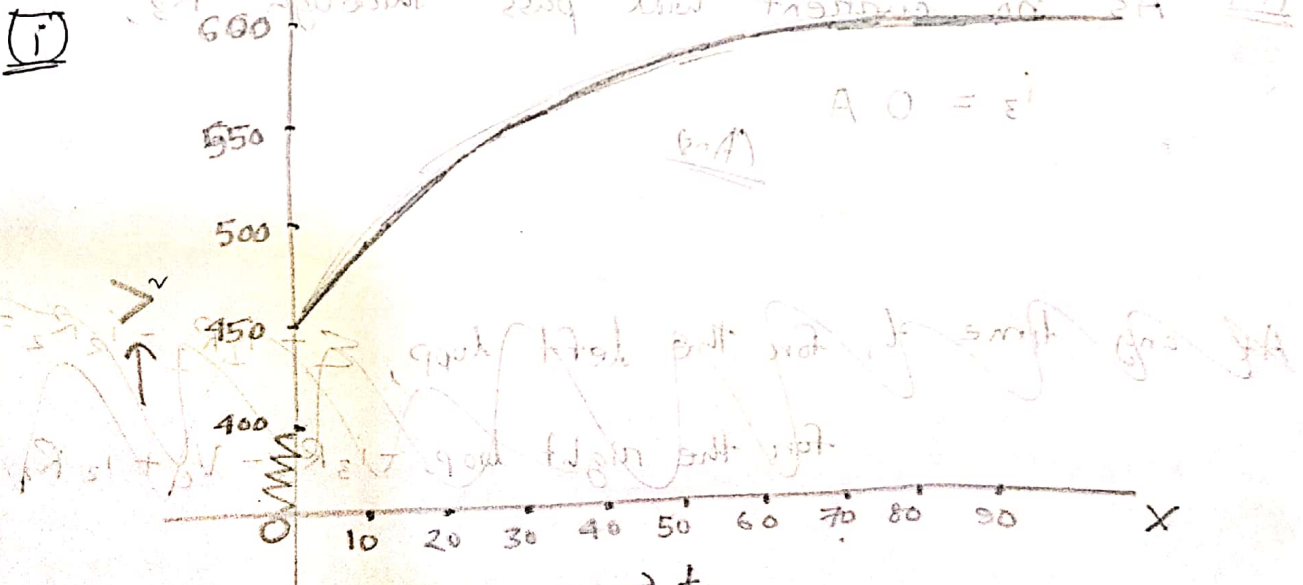


Fig:- V_2 vs t graph for R_2