

CSE 260 LAB Report

Experiment Name:- Parity Generator and
Checker

Submitted by :-

Name : Uday Saha

ID : 21301095

Section : 10

Date : 19 March, 2022


Objective:- To design and implement an Even Parity Generator and Even Parity checker using XOR gates (IC-7486).

Required Components and Equipments:-


1. AT-700 Portable Analog/Digital Laboratory
2. 7400 x 4
3. Wires

Experimental Setup:-

⊗ Even Parity Generator \Rightarrow

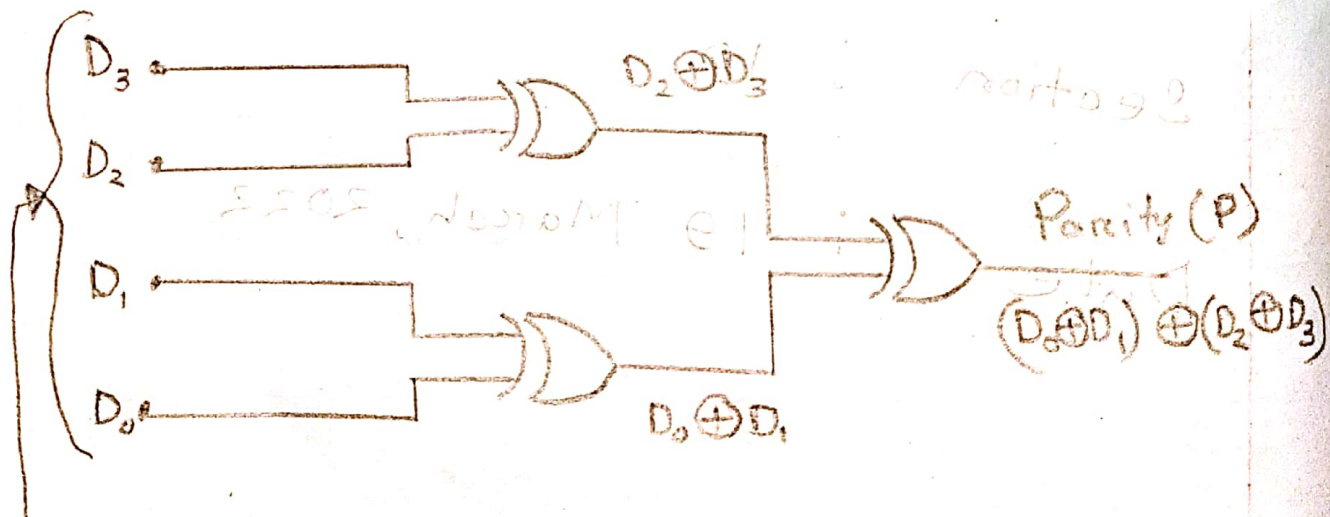

⊕ Even Parity Checker :-

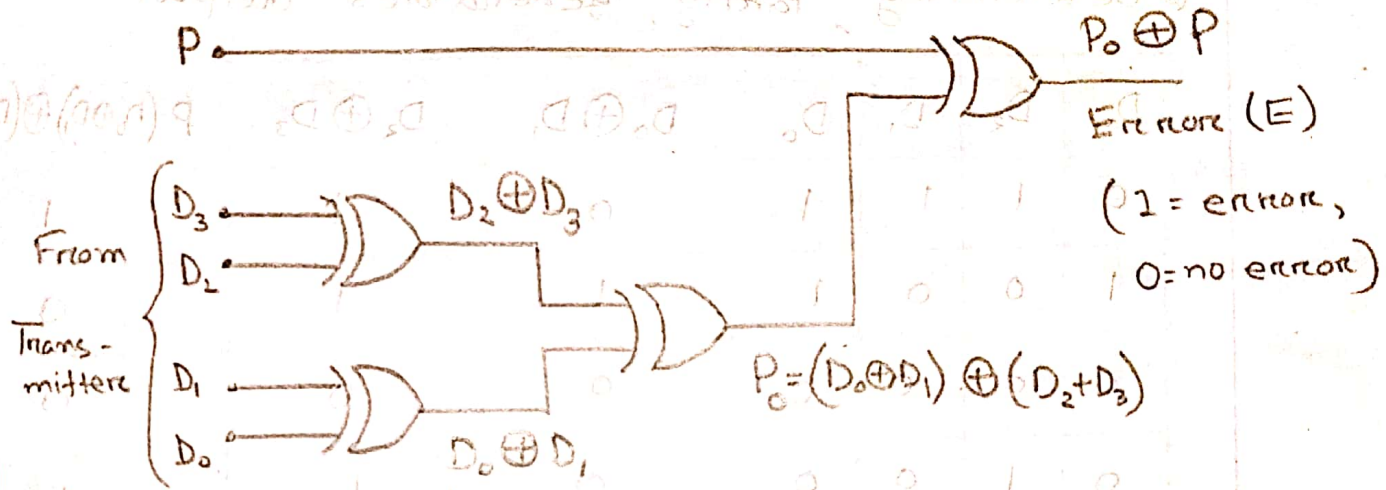

Now, we have to construct the figures on the bread-board of AT-700. We need to remember that, each IC's pin 14 is connected to '+5V' position of DC power supply of AT-700, and pin 7 is connected to 'GND' position. Now, connecting the inputs to Data Switches and outputs to any position of LED display, we need to generate the parity bit for \Rightarrow

a) 0111, b) 1001, c) 0000, d) 0100

And also check the parity for \Rightarrow

P	D_3	D_2	D_1	D_0
0	1	0	1	0
1	1	1	1	0
1	1	1	1	1
1	0	0	0	0

Result:-

⊗ Determining ^{Even} Parity generator's output

D_3	D_2	D_1	D_0	$D_0 \oplus D_1$	$D_2 \oplus D_3$	$P = (D_0 \oplus D_1) \oplus (D_2 \oplus D_3)$
0	1	1	1	0	1	1
1	0	0	1	1	1	0
0	0	0	0	0	0	0
0	1	0	0	0	1	1

⊗ Determining ^{Even} Parity checker's output

P	D_3	D_2	D_1	D_0	$D_0 \oplus D_1$	$D_2 \oplus D_3$	$P_0 = (D_0 \oplus D_1) \oplus (D_2 \oplus D_3)$	$E = P_0 \oplus P$
0	1	0	1	0	1	1	0	0
1	1	1	1	0	1	0	1	0
1	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	1

Discussion:-

While determining the Even Parity Generator's output, I have noticed that, whenever I have Even number of 1's in ~~by~~ my data, the Parity Bit is 0. For odd number 1's, the Parity Bit is 1 to make the number of 1's even.

Then, while checking the Even Parity Bit, I firstly generated the Parity for the transmitted data. Then I operated an X-OR operation with my derived Parity and the given Parity bit. Here, if the result is 0, there will be no error, meaning the Parity is correct. And 1 for otherwise. After getting the results, I got to know that for 1010 and 1110 there were no error. But there were errors for 1111 and 0000 in the given data, because their Parity Bits didn't match.