

CSE260 Lab Report

Experiment Name:-

Familiarization of Fundamental Logic Gates

Submitted by

Name : Uday Saha

ID : 21301095

Section : 10

Date : 21-02-22

Objective:-

① To get familiarized with fundamental logic gates and demonstrate the input output relationship of 2-input AND(IC-7408), OR (IC-7432) and NOT (IC-7404) gates by constructing their truth tables.

② To get familiarized with other logic gates like NAND(IC-7400), NOR(IC-7402), XOR(IC-7486) and XNOR(IC-74266).








Required Components and Equipments:-

Breadboard, wires, power, volt meter, various ICs, etc.

Experimental Setup:-

For conducting this experiment, we will need several ICs as follows - 7400, 7402, 7404, 7408, 7432, 7486, 74266. Their

pin layouts are given below.

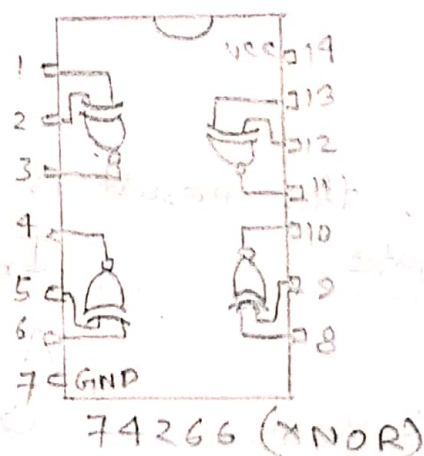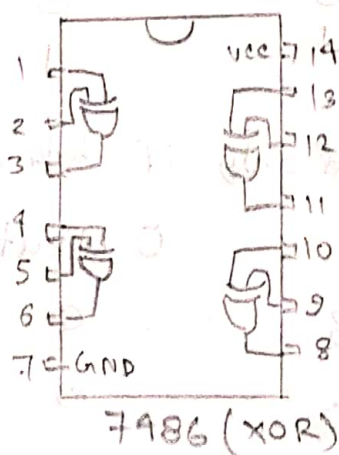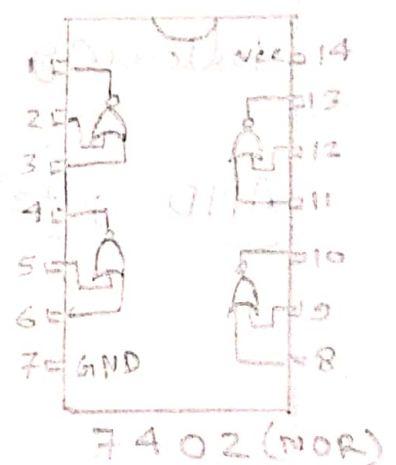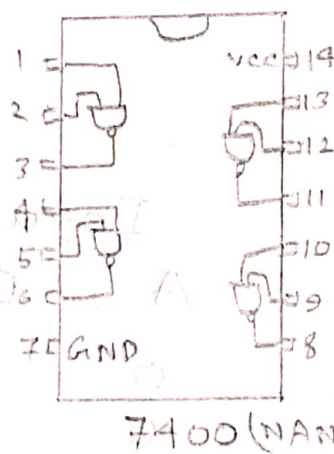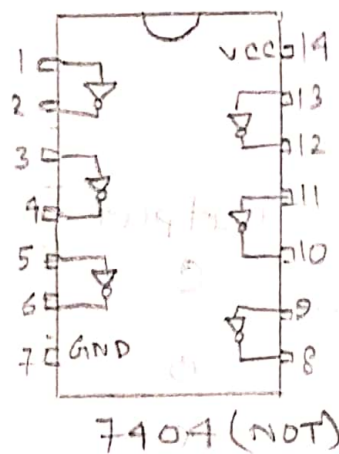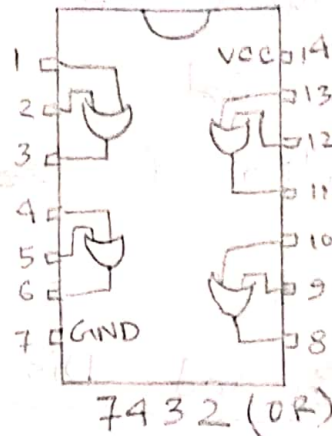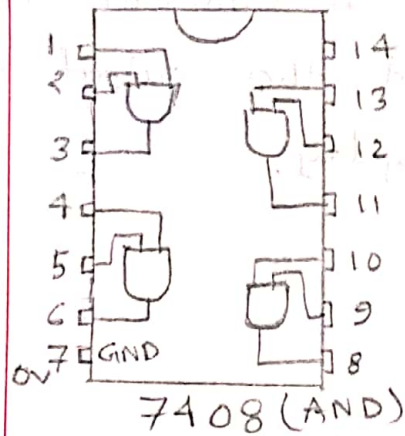

Here, we need to place the ICs on the trainer board. Then, connect pin 14 to +5V

position of DC power supply and pin 7 to GND position. Then we need to ~~to~~ connect the inputs to Data switches and the output to any position of the LED display.

Results and Discussions:-

The truth tables of the gates are as following:-

AND gate:-

Input		output
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Here, the result is True ~~if~~ only if both inputs are True

OR gate:-

Input		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Here, the result is True if at least 1 input is ~~False~~ True.

NOT gate:-

Input		Output
A	A	B
0	0	1
1	1	0

Here, the output is the ~~reverse~~ inverse of input.

NAND gate:-

Input		Output
A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Here, the gate is the combination of AND and NOT gate. The output is FALSE only if both the inputs are TRUE.

NOR gate:-

Input		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Here, the gate is the combination of OR and NOT gates. The output is TRUE only if both the inputs are FALSE.

XOR gate:-

Input		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

Here, the output is only TRUE when the inputs are opposite.

XNOR gate:-

Input		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

Here, the output is TRUE only when both the inputs are same.